

Course: CS-223 Digital Design
Section 01
Lab 03

Miray Ayerdem

21901987

08/03/2021

Trainer Pack Number: 28?

b) Behavioral SystemVerilog module for 2-to-4 decoder and a testbench for it.

```
module decoder2to4( input logic input1, input0,
                   output logic y3, y2, y1, y0);
    assign y3 = input1 & input0;
    assign y2 = input1 & ~input0;
    assign y1 = ~input1 & input0;
    assign y0 = ~input1 & ~input0;

endmodule
```

```
module testbench1();
    logic in1, in0;
    logic y3, y2, y1, y0;
    decoder2to4 testbench(in1, in0, y3, y2, y1, y0);
    initial begin
        in1 = 0; in0 = 0; #10;
        in0 = 1; #10;
        in1 = 1; in0 = 0; #10;
        in0 = 1; #10;
    end;
endmodule
```

c) Behavioral SystemVerilog module for 4-to-1 multiplexer.

```
module mux4to1(input logic input0, input1, input2, input3, s0, s1,
               output logic y);
    logic mux0, mux1;
    assign mux0 = s1 ? input1 : input0;
    assign mux1 = s1 ? input3 : input2;
    assign y = s0 ? mux1 : mux0;
endmodule
```

```
module testbench2();
    logic a, b, c, d, s0, s1, y;
    mux4to1 testbench(a, b, c, d, s0, s1, y);
    initial begin
        a = 0; b = 0; c = 0; d = 0; s0 = 0; s1 = 0; #10;
    end;
endmodule
```


[illegible]

```

a = 1; b = 1; c = 0; d = 0; s0 = 0; s1 = 1;#10;
a = 1; b = 1; c = 0; d = 0; s0 = 1; s1 = 0;#10;
a = 1; b = 1; c = 0; d = 0; s0 = 1; s1 = 1;#10;
a = 1; b = 1; c = 0; d = 1; s0 = 0; s1 = 0;#10;
a = 1; b = 1; c = 0; d = 1; s0 = 0; s1 = 1;#10;
a = 1; b = 1; c = 0; d = 1; s0 = 1; s1 = 0;#10;
a = 1; b = 1; c = 0; d = 1; s0 = 1; s1 = 1;#10;
a = 1; b = 1; c = 1; d = 0; s0 = 0; s1 = 0;#10;
a = 1; b = 1; c = 1; d = 0; s0 = 0; s1 = 1;#10;
a = 1; b = 1; c = 1; d = 0; s0 = 1; s1 = 0;#10;
a = 1; b = 1; c = 1; d = 0; s0 = 1; s1 = 1;#10;
a = 1; b = 1; c = 1; d = 1; s0 = 0; s1 = 0;#10;
a = 1; b = 1; c = 1; d = 1; s0 = 0; s1 = 1;#10;
a = 1; b = 1; c = 1; d = 1; s0 = 1; s1 = 0;#10;
a = 1; b = 1; c = 1; d = 1; s0 = 1; s1 = 1;#10;
end;
endmodule

```

 d) Schematic (block diagram) and structural System Verilog module of 8-to-1 MUX by using two 4-to-1 MUX modules, two AND gates, an INVERTER, and an OR gate and testbench for it.



```

module mux8to1(input logic input0, input1, input2, input3, input4, input5, input6, input7, s0,
s1, s2, output logic y);
    logic n0, n1, n2, n3, n4;
    mux4to1 mux0(input0, input2, input4, input6, s0, s1, n0);

```

```

mux4to1 mux1(input1, input3, input5, input7, s0, s1, n1);
not(n4, s2);
and( n2, n0, n4);
and(n3, s2, n1);
or( y, n3, n2);

```


```
endmodule
```

```

module testbench2();
  logic a, b, c, d, e, f, g, h, s0, s1, s2, y;
  mux8to1 testbench(a, b, c, d, e, f, g, h, s0, s1, s2, y);
  initial begin
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 0; s1 = 0; s2 = 0; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 0; s1 = 0; s2 = 1; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 0; s1 = 1; s2 = 0; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 0; s1 = 1; s2 = 1; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 1; s1 = 0; s2 = 0; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 1; s1 = 0; s2 = 1; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 1; s1 = 1; s2 = 0; #10;
    a = 0; b = 0; c = 1; d = 1; e = 0; f = 0; g = 1; h = 1; s0 = 1; s1 = 1; s2 = 1; #10;
  end
endmodule

```

 e) Schematic (block diagram) and SystemVerilog module for $F(A,B,C,D)=\sum(1,2,5,7,8,9,10,12,15)$ function, using one 8-to-1 multiplexer and an inverter.



```

module mux8to1min(input logic a, b, c, d, output logic y);
    mux8to1 mux(d, ~d, d, d, 1, ~d, ~d, d, a, b, c, y);
endmodule

```

```

module testbench3( );
    logic a,b,c,d,y;
    mux8to1min test(a,b,c,d,y);
    initial begin
        a = 0; b = 0; c = 0; d = 0;#10;
        a = 0; b = 0; c = 0; d = 1;#10;
        a = 0; b = 0; c = 1; d = 0;#10;
        a = 0; b = 0; c = 1; d = 1;#10;
        a = 0; b = 1; c = 0; d = 0;#10;
        a = 0; b = 1; c = 0; d = 1;#10;
        a = 0; b = 1; c = 1; d = 0;#10;
        a = 0; b = 1; c = 1; d = 1;#10;
        a = 1; b = 0; c = 0; d = 0;#10;
        a = 1; b = 0; c = 0; d = 1;#10;
        a = 1; b = 0; c = 1; d = 0;#10;
        a = 1; b = 0; c = 1; d = 1;#10;
        a = 1; b = 1; c = 0; d = 0;#10;
        a = 1; b = 1; c = 0; d = 1;#10;
        a = 1; b = 1; c = 1; d = 0;#10;
        a = 1; b = 1; c = 1; d = 1;#10;
    end
endmodule

```