

**Course: CS-223 Digital Design**  
**Section 01**  
**Lab 02**

Miray Ayerdem  
21901987  
25/02/2021

b) Schematic for a 1-bit fulladder


 


Fig 3: Full adder

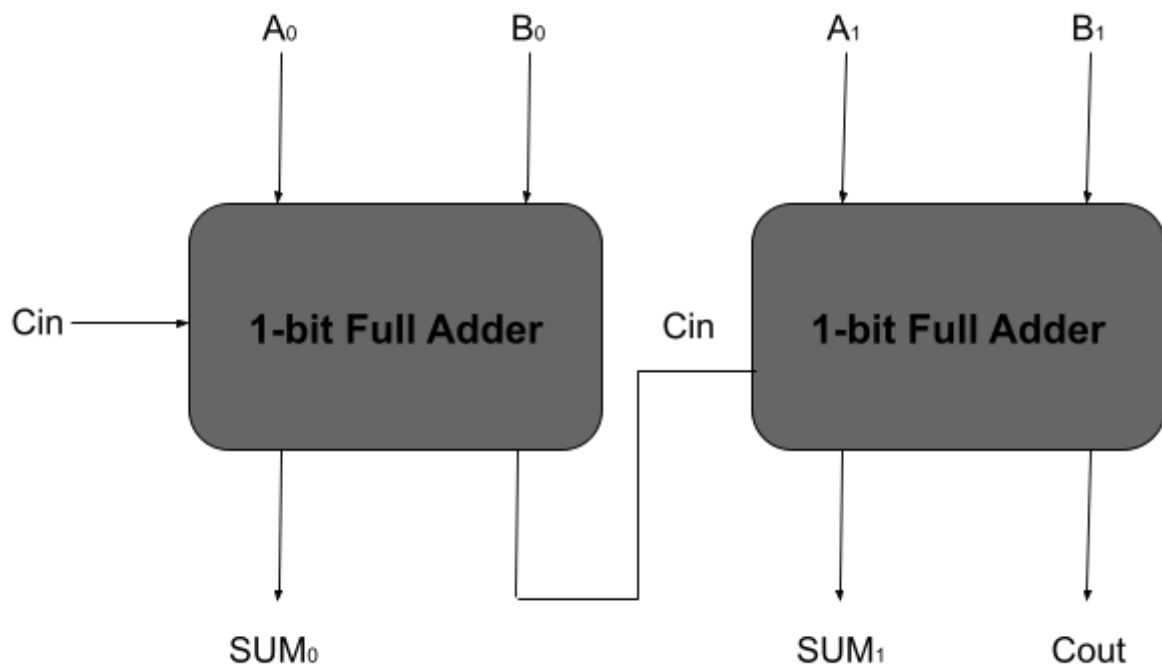c) Schematic for a 2-bit adder made from two 1-bit full adders



**d) Dataflow Systemverilog module for the 1-bit fulladder**

```
module fulladder(input logic x, y, z,
                 output logic sum, cout);
    assign sum = (x ^ y) ^ z;
    assign cout = (x & y) | ((x ^ y) & z);
endmodule
```

**e) Structural Systemverilog module for the 1-bit fulladder**

```
module xor2( input logic x, y,
             output logic z);
    assign z = x ^ y;
endmodule
```

```
module and2(input logic x, y,
            output logic z);
    assign z = x & y;
endmodule
```

```
module or2(input logic x, y,
           output logic z);
    assign z = x | y;
endmodule
```

```
module fulladder2( input logic a, b, cin,
                  output logic d, cout );
    logic n1, n2, n3;
    xor2 gatexor1(a, b, n1);
    xor2 gatexor2(n1, cin, d);
    and2 gateand1(a, b, n2);
    and2 gateand2(n1, cin, n3);
    or2 gateor(n2, n3, cout);
endmodule
```

**Testbench for the 1-bit fulladder**

```
module testbench();
    logic x, y, z;
    logic sum, cout;
    fulladder2 dut(x, y, z, sum, cout);
    initial begin
        x = 0; y = 0; z = 0; #10;
        x = 0; y = 0; z = 1; #10;
        x = 0; y = 1; z = 0; #10;
    end
endmodule
```

```

x = 0; y = 1; z = 1; #10;
x = 1; y = 1; z = 0; #10;
x = 1; y = 0; z = 0; #10;
x = 1; y = 0; z = 1; #10;
x = 1; y = 1; z = 1; #10;
end
endmodule

```

#### f) Structural Systemverilog module for the 2-bit adder

```

module fulladder2bit(input logic a0, b0, a1, b1, cin,
                    output logic sum0, sum1, cout);
    logic n1;
    fulladder2 fulladder1(a0, b0, cin, sum0, n1);
    fulladder2 fulladder2(a1, b1, n1, sum1, cout);
endmodule

```

#### Testbench for the 2-bit adder

```

module testbench2();
    logic x0, y0, x1, y1, cin, sum0, sum1, cout;
    fulladder2bit dut(x0, y0, x1, y1, cin, sum0, sum1, cout);
    initial begin
        x0 = 0; y0 = 0; cin = 0; x1 = 0; y1 = 0; #10;
        x0 = 0; y0 = 0; cin = 0; x1 = 0; y1 = 1; #10;
        x0 = 0; y0 = 0; cin = 0; x1 = 1; y1 = 0; #10;
        x0 = 0; y0 = 0; cin = 0; x1 = 1; y1 = 1; #10;
        x0 = 0; y0 = 0; cin = 1; x1 = 0; y1 = 0; #10;
        x0 = 0; y0 = 0; cin = 1; x1 = 0; y1 = 1; #10;
        x0 = 0; y0 = 0; cin = 1; x1 = 1; y1 = 0; #10;
        x0 = 0; y0 = 0; cin = 1; x1 = 1; y1 = 1; #10;
        x0 = 0; y0 = 1; cin = 0; x1 = 0; y1 = 0; #10;
        x0 = 0; y0 = 1; cin = 0; x1 = 0; y1 = 1; #10;
        x0 = 0; y0 = 1; cin = 0; x1 = 1; y1 = 0; #10;
        x0 = 0; y0 = 1; cin = 0; x1 = 1; y1 = 1; #10;
        x0 = 0; y0 = 1; cin = 1; x1 = 0; y1 = 0; #10;
        x0 = 0; y0 = 1; cin = 1; x1 = 0; y1 = 1; #10;
        x0 = 0; y0 = 1; cin = 1; x1 = 1; y1 = 0; #10;
        x0 = 0; y0 = 1; cin = 1; x1 = 1; y1 = 1; #10;
        x0 = 1; y0 = 0; cin = 0; x1 = 0; y1 = 0; #10;
        x0 = 1; y0 = 0; cin = 0; x1 = 0; y1 = 1; #10;
        x0 = 1; y0 = 0; cin = 0; x1 = 1; y1 = 0; #10;
        x0 = 1; y0 = 0; cin = 0; x1 = 1; y1 = 1; #10;
        x0 = 1; y0 = 0; cin = 1; x1 = 0; y1 = 0; #10;
        x0 = 1; y0 = 0; cin = 1; x1 = 0; y1 = 1; #10;
        x0 = 1; y0 = 0; cin = 1; x1 = 1; y1 = 0; #10;
        x0 = 1; y0 = 0; cin = 1; x1 = 1; y1 = 1; #10;
        x0 = 1; y0 = 1; cin = 0; x1 = 0; y1 = 0; #10;
    end
endmodule

```

```
x0 = 1; y0 = 1; cin = 0; x1 = 0; y1 = 1; #10;  
x0 = 1; y0 = 1; cin = 0; x1 = 1; y1 = 0; #10;  
x0 = 1; y0 = 1; cin = 0; x1 = 1; y1 = 1; #10;  
x0 = 1; y0 = 1; cin = 1; x1 = 0; y1 = 0; #10;  
x0 = 1; y0 = 1; cin = 1; x1 = 0; y1 = 1; #10;  
x0 = 1; y0 = 1; cin = 1; x1 = 1; y1 = 0; #10;  
x0 = 1; y0 = 1; cin = 1; x1 = 1; y1 = 1; #10;  
end  
endmodule
```